

$\text{Fault} \Rightarrow \left\{ \begin{array}{l} 1 \text{ line to ground} \\ 2 \text{ lines to ground} \\ 1 \text{ line to 1 line} \\ 3 \text{ lines together} \end{array} \right.$

$\text{open} \left\{ \begin{array}{l} 1 \text{ conductor open} \\ 2 \text{ conductor open} \end{array} \right.$

load current \ll fault current \Rightarrow


omit load current

V_{source} no change

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_0 + V_1 + V_2 \\ \dots \\ \dots \end{bmatrix}$$

1 line to ground

70%

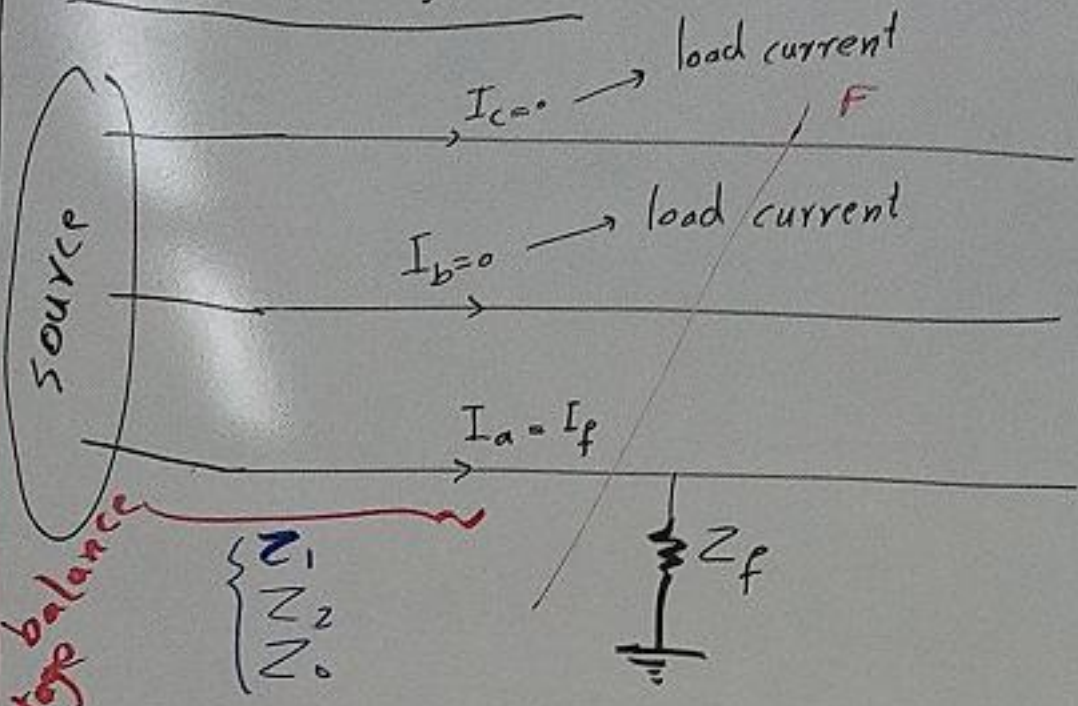

F: $\{V_a, V_b, V_c\}$
unbalance

faulted phase = a

voltage balance

$\begin{cases} Z_1 \\ Z_2 \\ Z_0 \end{cases}$

$$V_a = Z_f I_a$$

$$\begin{bmatrix} I_0 \\ I_1 \\ I_r \end{bmatrix} = \frac{1}{\sqrt{3}} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^r \\ 1 & a^r & a \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix} = \frac{1}{\sqrt{3}} \begin{bmatrix} I_a \\ I_a \\ I_a \end{bmatrix}$$

$$I_0 = I_1 = I_r = \frac{1}{\sqrt{3}} I_a$$


$$I_0 = I_1 = I_2$$

$$V_a = V_0 + V_1 + V_2$$

$$V_a = V_0 + V_1 + V_2$$

$$V_0 + V_1 + V_2 = 3Z_f I_f$$

balance

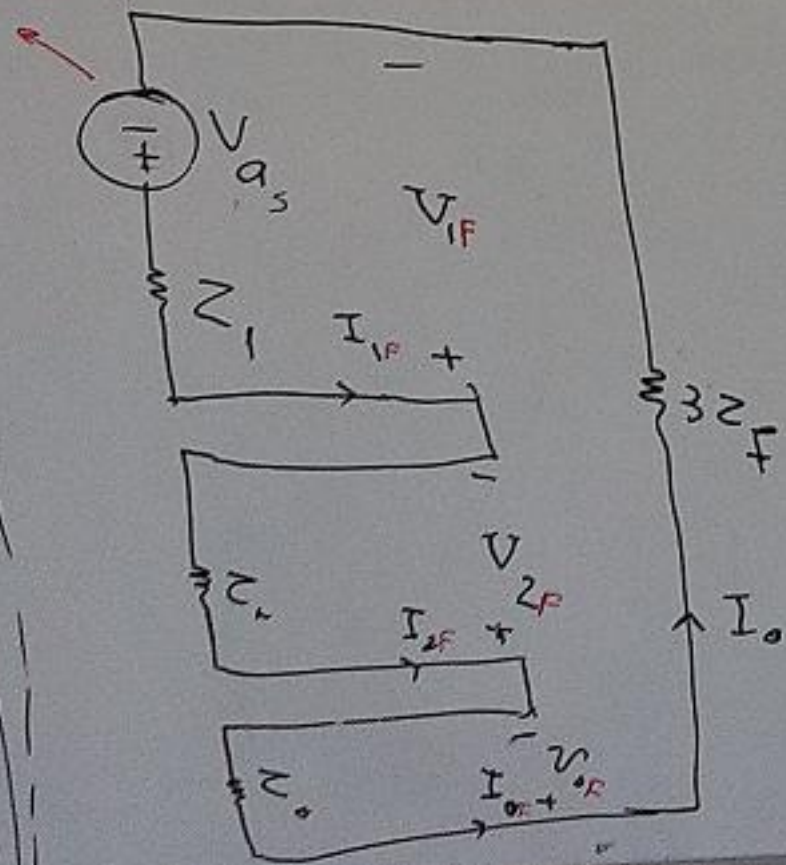


$$I_0 = I_1 = I_r = \frac{V_a}{Z_1 + Z_r + Z_2 + 3Z_f}$$

$$I_a = \frac{3V_a}{Z_1 + Z_r + Z_2 + 3Z_f}$$

$$\begin{cases} V_1 = V_a - Z_1 I_1 \\ V_2 = -Z_2 I_2 \\ V_0 = -Z_0 I_0 \end{cases} \Rightarrow \begin{cases} V_a \\ V_b \\ V_c \end{cases}$$

2 lines to ground



1.1

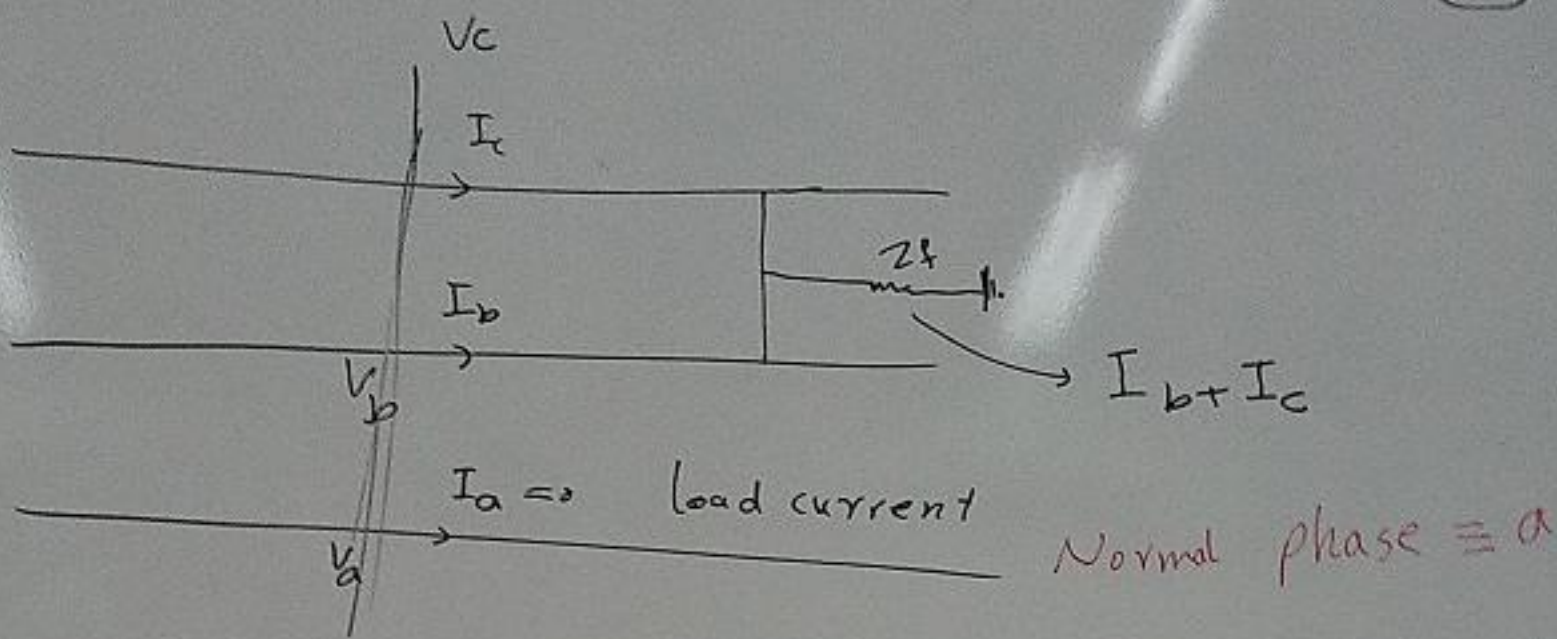


$$V_c = V_b = Z_f (I_b + I_c)$$

$$\begin{cases} I_1 + I_2 + I_0 = 0 \end{cases}$$
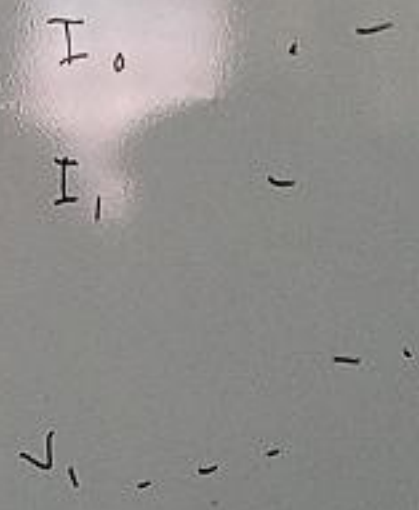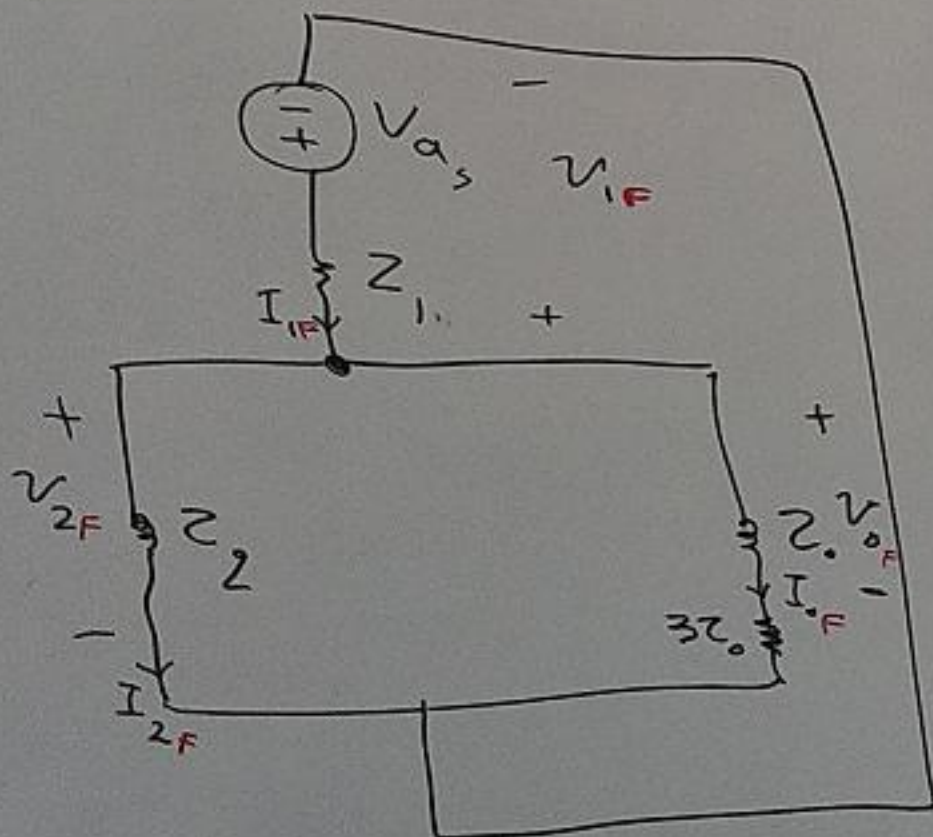
$$\begin{cases} V_1 = V_2, V_0 = V_1 + 3Z_0 I_0 \end{cases}$$




1 line to 1 line

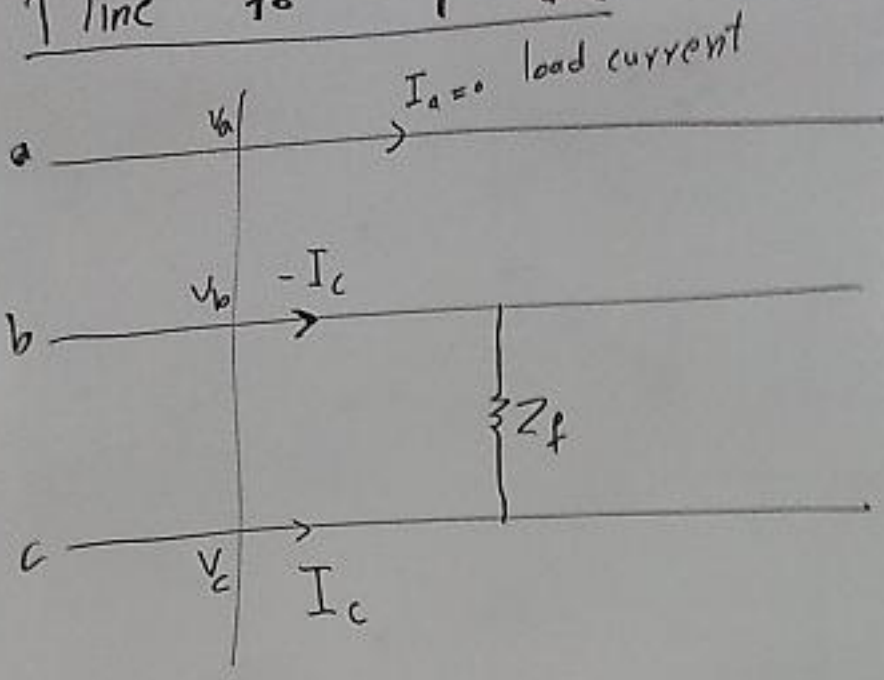

Normal phase $\equiv \phi$

$$V_c - V_b = Z_f I_c, \quad I_b = -I_c$$
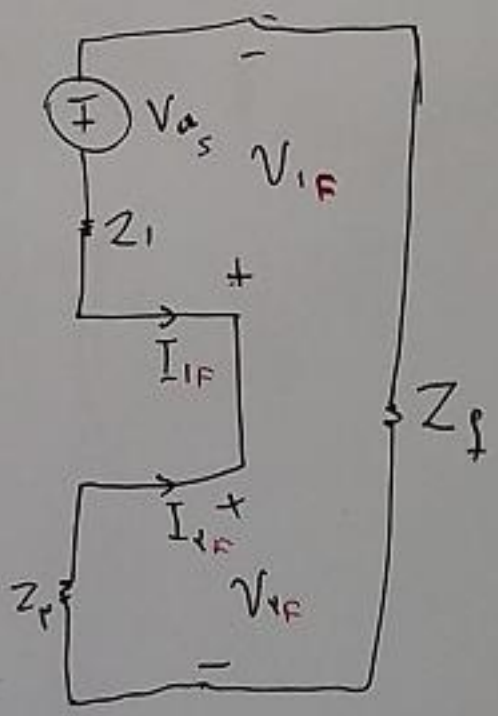
$$\begin{cases} I_0 = 0, \quad I_r = -I_1 \\ V_1 - V_2 = Z_f I_1, \quad V_1 = V_2 \end{cases}$$



- I_0
- I_1
- V_1
- V_2
- V_a
- V_b