
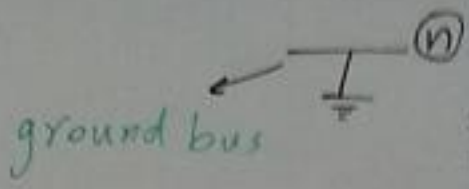
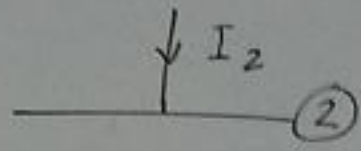


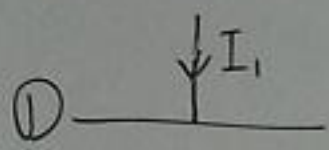Chapter 3: (s.c. calculation using matrices)



$$\begin{bmatrix} I_1 \\ I_2 \\ I_r \\ \vdots \\ I_{n-1} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1(n-1)} \\ Y_{21} & Y_{22} & \dots & Y_{2(n-1)} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{(n-1)1} & \dots & \dots & Y_{(n-1)(n-1)} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_{n-1} \end{bmatrix}$$

(I_i : current source)

$$Y_{bus} \Rightarrow \underline{I} = Y_{bus} \underline{v}$$

$$Z_{bus} = Y_{bus}^{-1} \Rightarrow \underline{v} = Z_{bus} \underline{i}$$

Y_{bus} calculation:

① solution:

General: $Y_{ii} = \left\{ \begin{array}{l} \text{the summation of admittances} \\ \text{which are connected to bus } i \end{array} \right.$

$Y_{ij} = - \left\{ \begin{array}{l} \text{the summation of admittances} \\ \text{which are between bus } i \text{ \& bus } j \end{array} \right.$

solution 2:

② $Y_{ij} = \frac{I_i}{V_j} \Big/ (V_1, V_2, \dots, V_{j-1}, V_{j+1}, \dots, V_n) = 0$

calculated

source

Z_{bus} calculation:

① solution:

$$Y_{bus}^{-1}$$

② solution:

$Z_{ij} = \frac{V_i}{I_j} \Big/ (I_1, I_2, \dots, I_{j-1}, I_{j+1}, \dots, I_n) = 0$

calculated

source



(open circuit test)

③ solution: step-by-step formation.

3.7.1 \rightarrow 3.7.5

④ graph theory: (next session)

$$Z_{bus} =$$

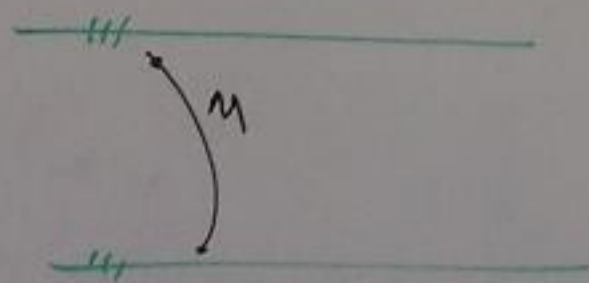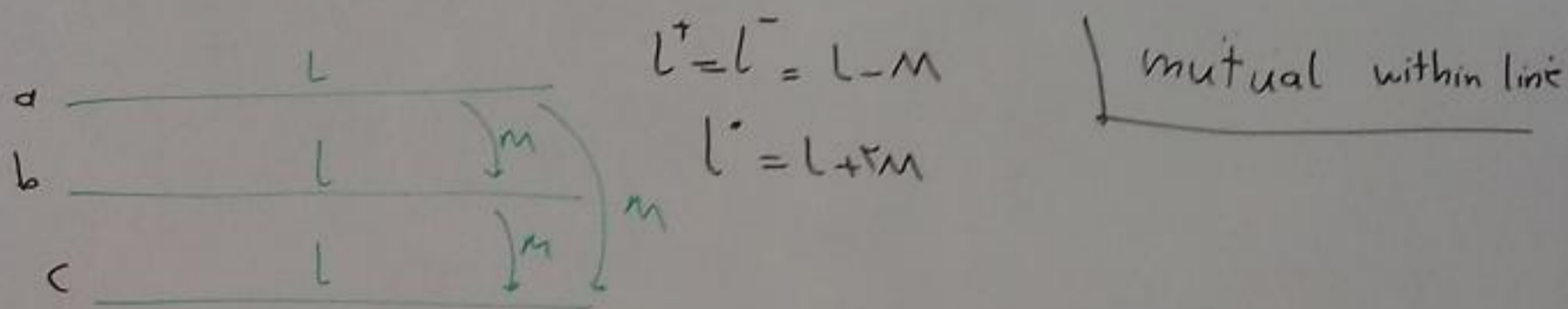


mutual between lines

S.C. calculation using Z_{bus}

Solution 1: (other books)

$$i_{load} = 0$$

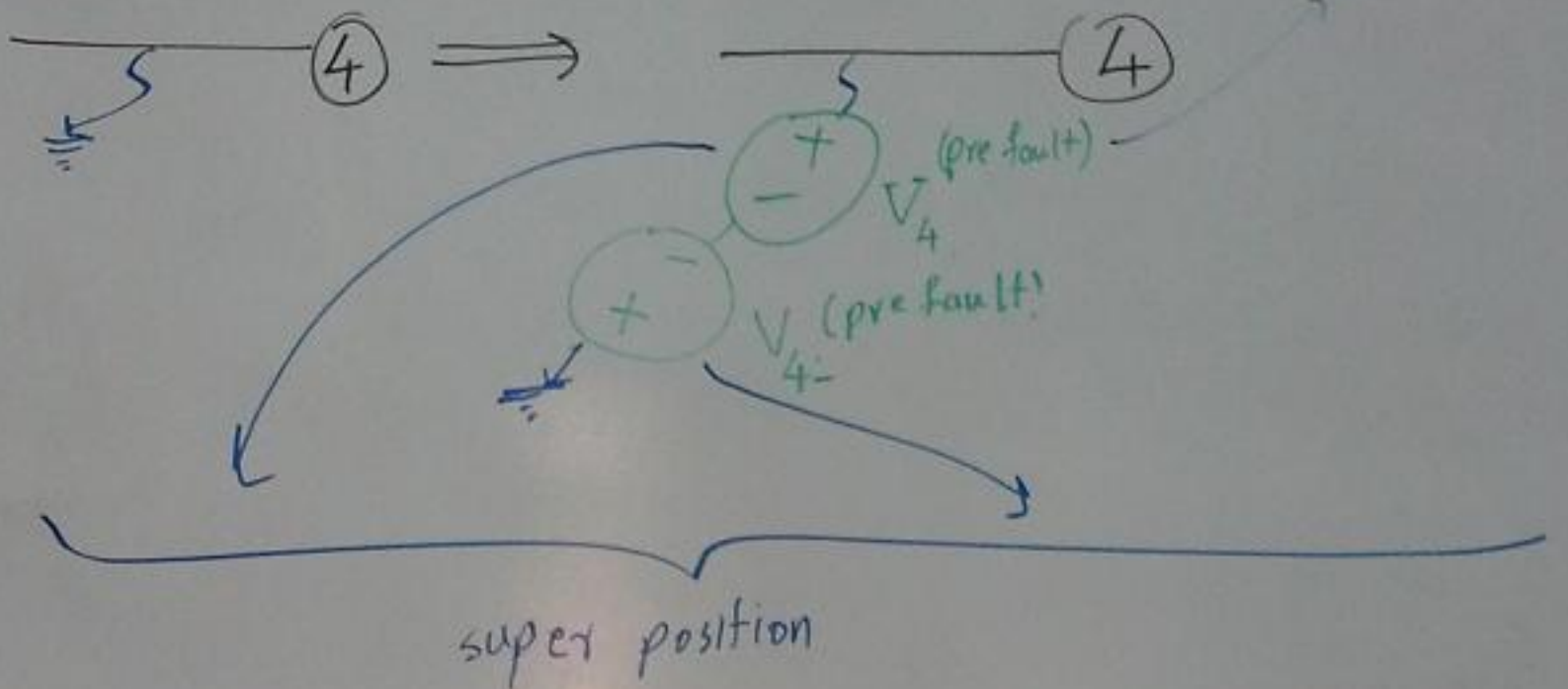

All generators + $(V_4 \text{ pre-fault})$

{ All generators \Rightarrow open circuit
+ $V_{4-} \text{ pre-fault}$

{ Connect voltage source
to the bus which is equal
to voltage bus

$$V_{4-} \text{ (pre-fault)} = -V_4 \text{ (pre-fault)} = -Z_{44} I_4 \text{ pre-fault}$$

$$I_4 = -\frac{V_4 \text{ pre-fault}}{Z_{44}}$$

\Downarrow
no impact on the network

$$I_4 = 0$$

$$\Rightarrow I_4 = \frac{-V_4^{(\text{prefault})}}{Z_{44}} = -\frac{1}{Z_{44}} \Rightarrow I_{sc} = \frac{1}{Z_{44}}$$

↓
injected